

Inhaltsverzeichnis

1. TCE Tinycore Linux Project englisch	11
2. Benutzer:OE2WAO	5
3. Geeignete Soundkarten	8
4. TCE Tinycore Linux Projekt	14

TCE Tinycore Linux Project englisch

Versionsgeschichte interaktiv durchsuchen
VisuellWikitext

Version vom 9. März 2015, 17:08 Uhr (Quelltext anzeigen)
OE2WAO ([Diskussion](#) | [Beiträge](#))
([→Help](#))
[← Zum vorherigen Versionsunterschied](#)

Version vom 7. August 2020, 09:51 Uhr (Quelltext anzeigen)
OE2WAO ([Diskussion](#) | [Beiträge](#))
[K](#)
[Zum nächsten Versionsunterschied →](#)

Zeile 1:

==Intro==
[[Bild:PPC.jpg|thumb|500MHz LowPower industrial PC]]

Zeile 1:

+
[[Datei:Deutschland-flagge.gif]] Für die deutsche Version dieses Projekts
[[TCE Tinycore_Linux_Projekt | >>hier klicken<<]]
==Intro==
[[Bild:PPC.jpg|thumb|500MHz LowPower industrial PC]]

Version vom 7. August 2020, 09:51 Uhr

 Für die deutsche Version dieses Projekts [>>hier klicken<<](#)

Inhaltsverzeichnis

1	Intro	12
2	Hardware	12
2.1	Connections and conversion of the used industrial pc	12
2.2	Soundcard	13
3	Software	13
3.1	Software schematic	13
4	Help	13

Intro


This hamradio software project is based on [TCE - Tinycore Linux](#), an embedded software system used on platforms like industrial pc, ALIX and others, and offers services and possibilities like

- packet radio,
- BBS,
- APRS,
- lightning log,
- small webserver,
- SVX-Link (Echolink)

especialy in networks like HAMNET and similar.

One goal is a minimum on material expenditure and also a minimal current consumption, followed by a maximum of features

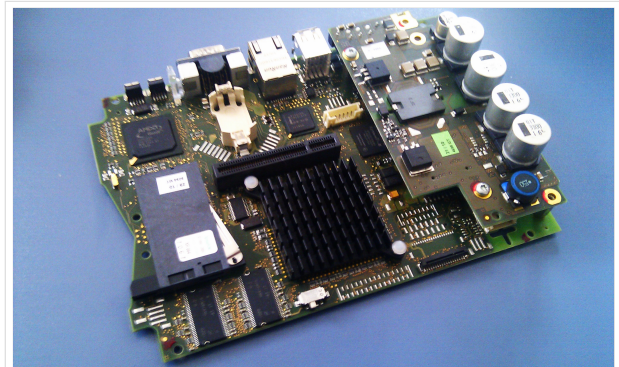More information on the hamradio TCE - tinycore linux project coming here soon




500MHz LowPower industrial PC

Hardware

DH2IW Wolfgang, OE2WAO Mike and OE5DXL Chris are doing first experiments with discarded industrial pc hardware, a 500MHz AMD Geode CPU with up to 256MB of RAM, and a minimal power input of <5Watt (for remaining stock ask [OE2WAO](#)).

But every other hardware platform like ALIX or similar will do.

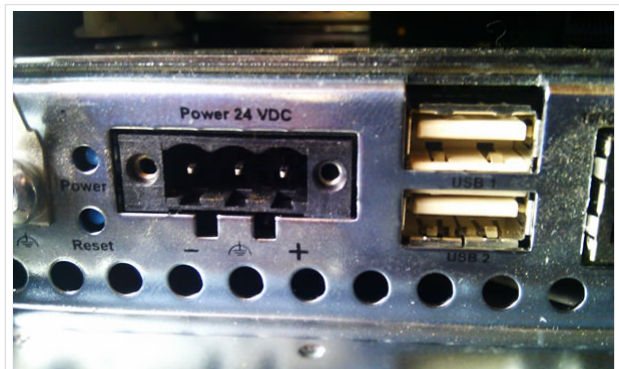The operating system is placed on a CF memory card (>32MB).



polarity industrial PC


A USB soundcard is used for operating AFSK /FSK modulation. One special character of working devices is a 3rd connector beside microphone and line out, the line in. Because these device are real stereo and make it possible to operate two separate channels on one sound card.

Connections and conversion of the used industrial pc

There are several connectors (COM, USB, network) on the frontside of our panels, as you can see. For correct polarity it is important to connent the + pole to the right pin of the 3pol power supply connector, the pin which is closer to the USB ports. The negative pole is the left pin.

The normal board supply is 24V.

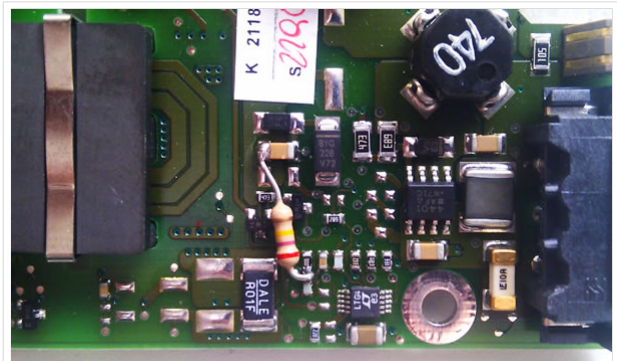That we can use it with our 12V power supply, we have to do a little modification. Just add a 270k Ohm resistor on the bottom side of the power supply as shown in the picture.



power supply conversion 12V

Soundcard


If there is no onboard sound available, you can use a USB soundcard instead. Suggested types you can find [here](#).

Software

A ready-to-use software image is located on the [OE2WAO Server](#) (e.g. tc455x-128.zip means version 4.55 with GUI on 128MB data drive)

There is also a version for raspberry pi hardware in test, and available soon.

Software schematic

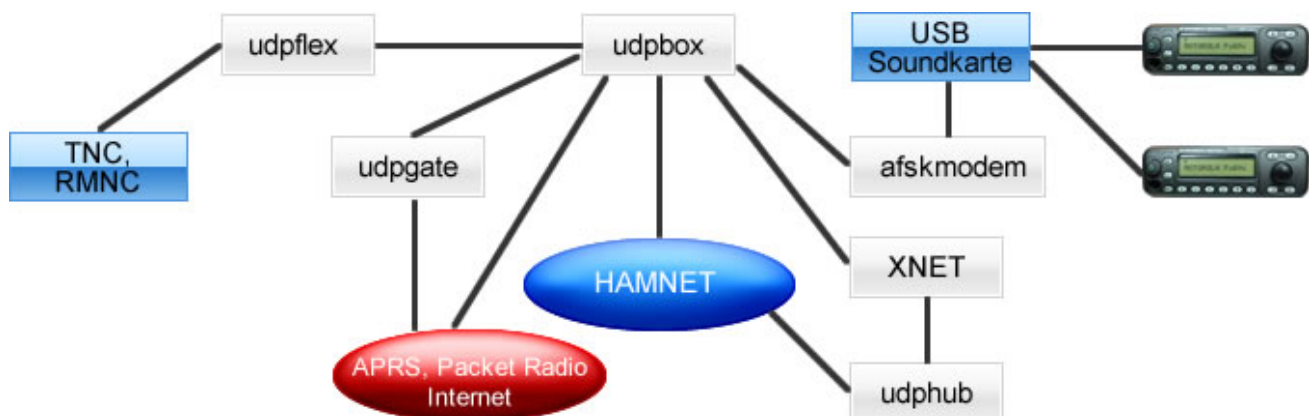

Help

If you need help on configuring the software packages you can contact OE5DXL on packet radio convers channel 501.

TCE Tinycore Linux Project englisch: Unterschied zwischen den Versionen

[Versionsgeschichte interaktiv durchsuchen](#)
[Visuell Wikitext](#)

Version vom 9. März 2015, 17:08 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
([→Help](#))
[← Zum vorherigen Versionsunterschied](#)

Version vom 7. August 2020, 09:51 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
[K](#)
[Zum nächsten Versionsunterschied →](#)

Zeile 1:	Zeile 1:
	[[Datei:Deutschland-flagge.gif]] Für die deutsche Version dieses Projekts [[TCE Tinycore Linux Projekt >>hier klicken<<]]
==Intro==	==Intro==
[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]	[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]

Version vom 7. August 2020, 09:51 Uhr

 Für die deutsche Version dieses Projekts [>>hier klicken<<](#)

Inhaltsverzeichnis

1	Intro	6
2	Hardware	6
2.1	Connections and conversion of the used industrial pc	6
2.2	Soundcard	7
3	Software	7
3.1	Software schematic	7
4	Help	7

Intro


This hamradio software project is based on [TCE - Tinycore Linux](#), an embedded software system used on platforms like industrial pc, ALIX and others, and offers services and possibilities like

- packet radio,
- BBS,
- APRS,
- lightning log,
- small webserver,
- SVX-Link (Echolink)

especialy in networks like HAMNET and similar.

One goal is a minimum on material expenditure and also a minimal current consumption, followed by a maximum of features

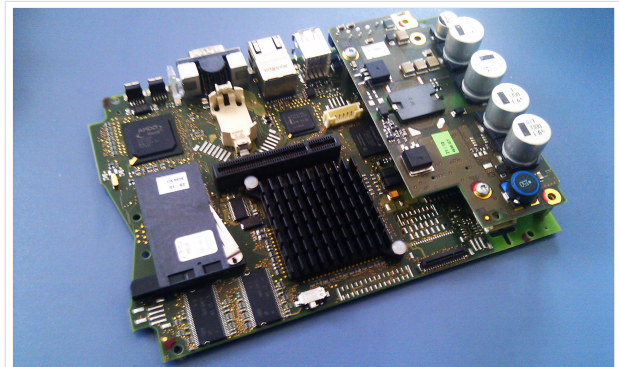More information on the hamradio TCE - tinycore linux project coming here soon




500MHz LowPower industrial PC

Hardware

DH2IW Wolfgang, OE2WAO Mike and OE5DXL Chris are doing first experiments with discarded industrial pc hardware, a 500MHz AMD Geode CPU with up to 256MB of RAM, and a minimal power input of <5Watt (for remaining stock ask [OE2WAO](#)).

But every other hardware platform like ALIX or similar will do.

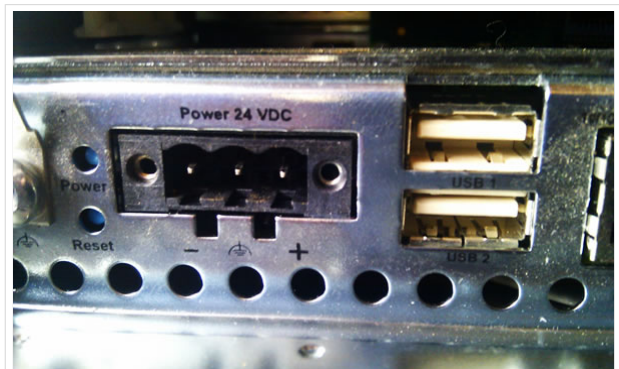The operating system is placed on a CF memory card (>32MB).



polarity industrial PC


A USB soundcard is used for operating AFSK /FSK modulation. One special character of working devices is a 3rd connector beside microphone and line out, the line in. Because these device are real stereo and make it possible to operate two separate channels on one sound card.

Connections and conversion of the used industrial pc

There are several connectors (COM, USB, network) on the frontside of our panels, as you can see. For correct polarity it is important to connent the + pole to the right pin of the 3pol power supply connector, the pin which is closer to the USB ports. The negative pole is the left pin.

The normal board supply is 24V.

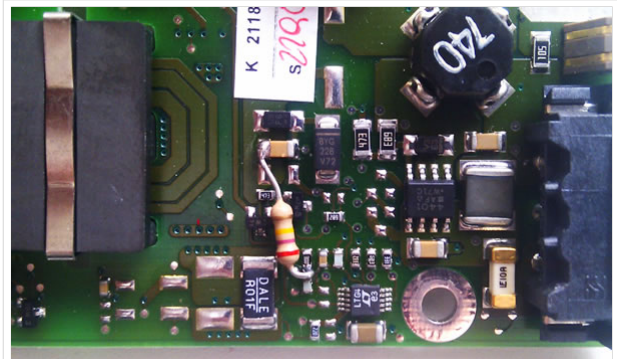That we can use it with our 12V power supply, we have to do a little modification. Just add a 270k Ohm resistor on the bottom side of the power supply as shown in the picture.



power supply conversion 12V

Soundcard


If there is no onboard sound available, you can use a USB soundcard instead. Suggested types you can find [here](#).

Software

A ready-to-use software image is located on the [OE2WAO Server](#) (e.g. tc455x-128.zip means version 4.55 with GUI on 128MB data drive)

There is also a version for raspberry pi hardware in test, and available soon.

Software schematic

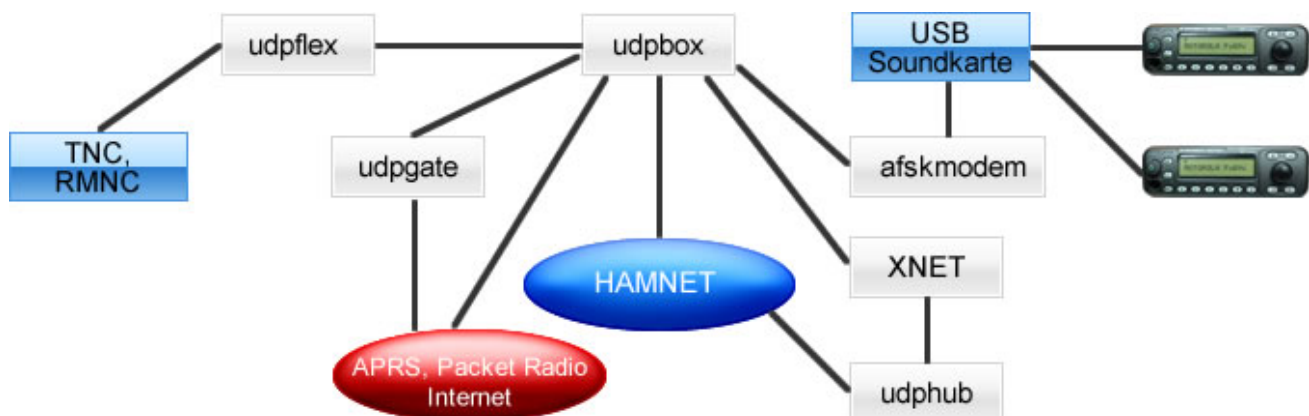

Help

If you need help on configuring the software packages you can contact OE5DXL on packet radio convers channel 501.

TCE Tinycore Linux Project englisch: Unterschied zwischen den Versionen

[Versionsgeschichte interaktiv durchsuchen](#)
[Visuell Wikitext](#)

Version vom 9. März 2015, 17:08 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
([→Help](#))
[← Zum vorherigen Versionsunterschied](#)

Version vom 7. August 2020, 09:51 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
[K](#)
[Zum nächsten Versionsunterschied →](#)

Zeile 1:	Zeile 1:
	[[Datei:Deutschland-flagge.gif]] Für die deutsche Version dieses Projekts [[TCE Tinycore Linux Projekt >>hier klicken<<]]
==Intro==	==Intro==
[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]	[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]

Version vom 7. August 2020, 09:51 Uhr

 Für die deutsche Version dieses Projekts [>>hier klicken<<](#)

Inhaltsverzeichnis

1	Intro	9
2	Hardware	9
2.1	Connections and conversion of the used industrial pc	9
2.2	Soundcard	10
3	Software	10
3.1	Software schematic	10
4	Help	10

Intro


This hamradio software project is based on [TCE - Tinycore Linux](#), an embedded software system used on platforms like industrial pc, ALIX and others, and offers services and possibilities like

- packet radio,
- BBS,
- APRS,
- lightning log,
- small webserver,
- SVX-Link (Echolink)

especialy in networks like HAMNET and similar.

One goal is a minimum on material expenditure and also a minimal current consumption, followed by a maximum of features

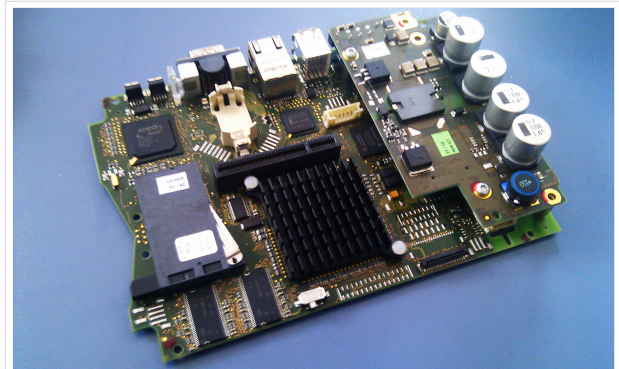More information on the hamradio TCE - tinycore linux project coming here soon




500MHz LowPower industrial PC

Hardware

DH2IW Wolfgang, OE2WAO Mike and OE5DXL Chris are doing first experiments with discarded industrial pc hardware, a 500MHz AMD Geode CPU with up to 256MB of RAM, and a minimal power input of <5Watt (for remaining stock ask [OE2WAO](#)).

But every other hardware platform like ALIX or similar will do.

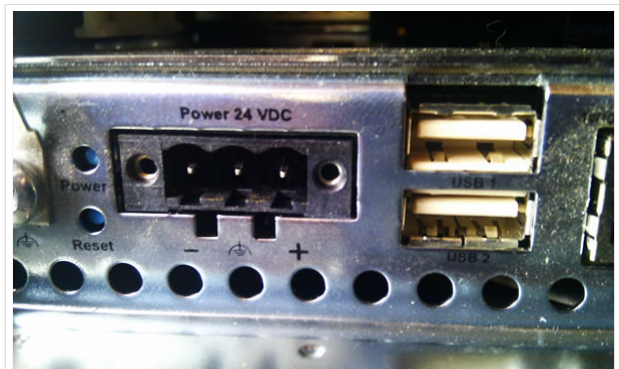The operating system is placed on a CF memory card (>32MB).



polarity industrial PC


A USB soundcard is used for operating AFSK /FSK modulation. One special character of working devices is a 3rd connector beside microphone and line out, the line in. Because these device are real stereo and make it possible to operate two separate channels on one sound card.

Connections and conversion of the used industrial pc

There are several connectors (COM, USB, network) on the frontside of our panels, as you can see. For correct polarity it is important to connent the + pole to the right pin of the 3pol power supply connector, the pin which is closer to the USB ports. The negative pole is the left pin.

The normal board supply is 24V.

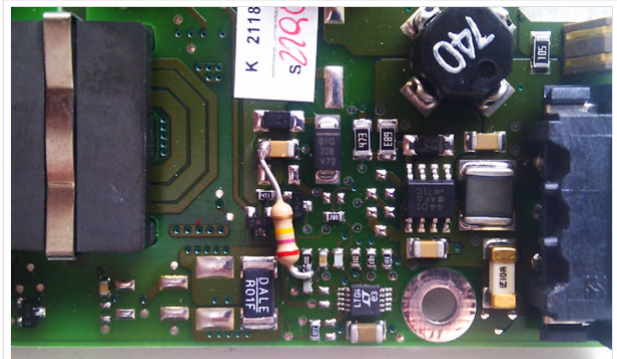That we can use it with our 12V power supply, we have to do a little modification. Just add a 270k Ohm resistor on the bottom side of the power supply as shown in the picture.



power supply conversion 12V

Soundcard


If there is no onboard sound available, you can use a USB soundcard instead. Suggested types you can find [here](#).

Software

A ready-to-use software image is located on the [OE2WAO Server](#) (e.g. tc455x-128.zip means version 4.55 with GUI on 128MB data drive)

There is also a version for raspberry pi hardware in test, and available soon.

Software schematic

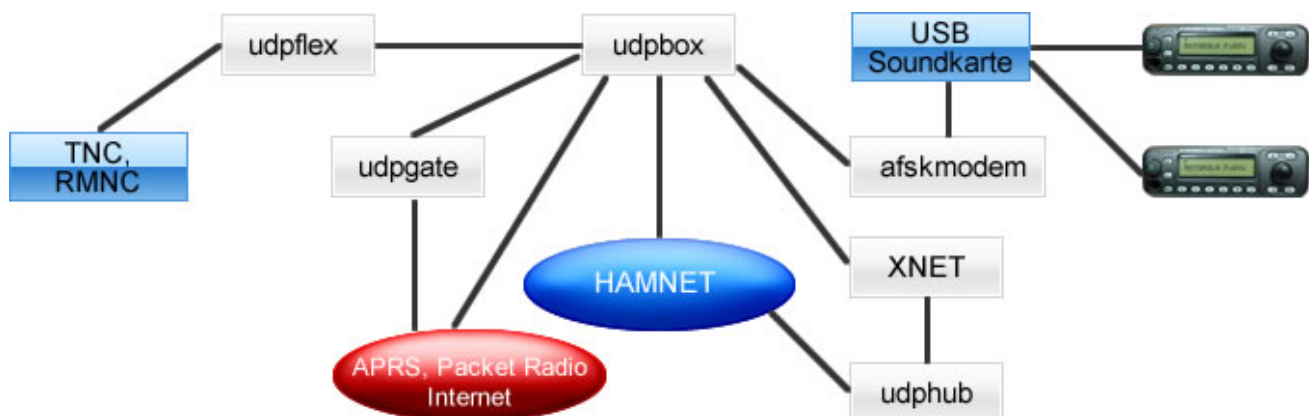

Help

If you need help on configuring the software packages you can contact OE5DXL on packet radio convers channel 501.

TCE Tinycore Linux Project englisch: Unterschied zwischen den Versionen

[Versionsgeschichte interaktiv durchsuchen](#)
[Visuell Wikitext](#)

Version vom 9. März 2015, 17:08 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
([→Help](#))
[← Zum vorherigen Versionsunterschied](#)

Version vom 7. August 2020, 09:51 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
[K](#)
[Zum nächsten Versionsunterschied →](#)

Zeile 1:	Zeile 1:
	[[Datei:Deutschland-flagge.gif]] Für die deutsche Version dieses Projekts [[TCE Tinycore Linux Projekt >>hier klicken<<]]
==Intro==	==Intro==
[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]	[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]

Version vom 7. August 2020, 09:51 Uhr

 Für die deutsche Version dieses Projekts [>>hier klicken<<](#)

Inhaltsverzeichnis

1	Intro	12
2	Hardware	12
2.1	Connections and conversion of the used industrial pc	12
2.2	Soundcard	13
3	Software	13
3.1	Software schematic	13
4	Help	13

Intro


This hamradio software project is based on [TCE - Tinycore Linux](#), an embedded software system used on platforms like industrial pc, ALIX and others, and offers services and possibilities like

- packet radio,
- BBS,
- APRS,
- lightning log,
- small webserver,
- SVX-Link (Echolink)

especialy in networks like HAMNET and similar.

One goal is a minimum on material expenditure and also a minimal current consumption, followed by a maximum of features

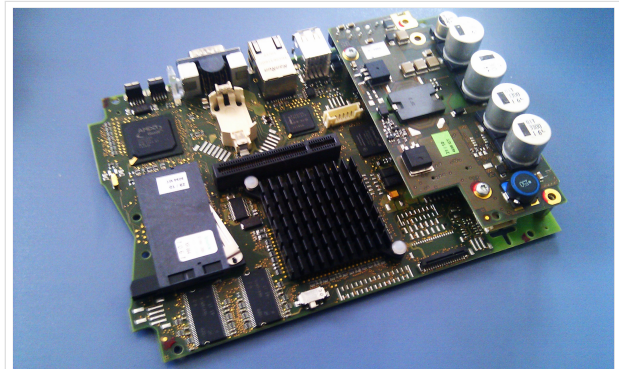More information on the hamradio TCE - tinycore linux project coming here soon




500MHz LowPower industrial PC

Hardware

DH2IW Wolfgang, OE2WAO Mike and OE5DXL Chris are doing first experiments with discarded industrial pc hardware, a 500MHz AMD Geode CPU with up to 256MB of RAM, and a minimal power input of <5Watt (for remaining stock ask [OE2WAO](#)).

But every other hardware platform like ALIX or similar will do.

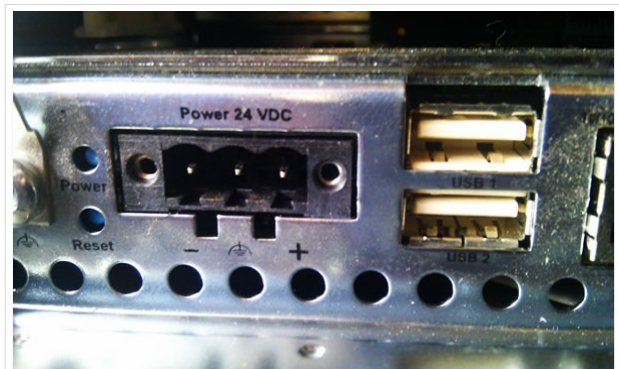The operating system is placed on a CF memory card (>32MB).



polarity industrial PC


A USB soundcard is used for operating AFSK /FSK modulation. One special character of working devices is a 3rd connector beside microphone and line out, the line in. Because these device are real stereo and make it possible to operate two separate channels on one sound card.

Connections and conversion of the used industrial pc

There are several connectors (COM, USB, network) on the frontside of our panels, as you can see. For correct polarity it is important to connent the + pole to the right pin of the 3pol power supply connector, the pin which is closer to the USB ports. The negative pole is the left pin.

The normal board supply is 24V.

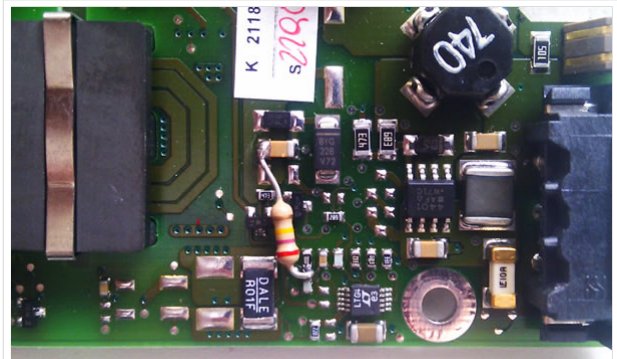That we can use it with our 12V power supply, we have to do a little modification. Just add a 270k Ohm resistor on the bottom side of the power supply as shown in the picture.



power supply conversion 12V

Soundcard


If there is no onboard sound available, you can use a USB soundcard instead. Suggested types you can find [here](#).

Software

A ready-to-use software image is located on the [OE2WAO Server](#) (e.g. tc455x-128.zip means version 4.55 with GUI on 128MB data drive)

There is also a version for raspberry pi hardware in test, and available soon.

Software schematic

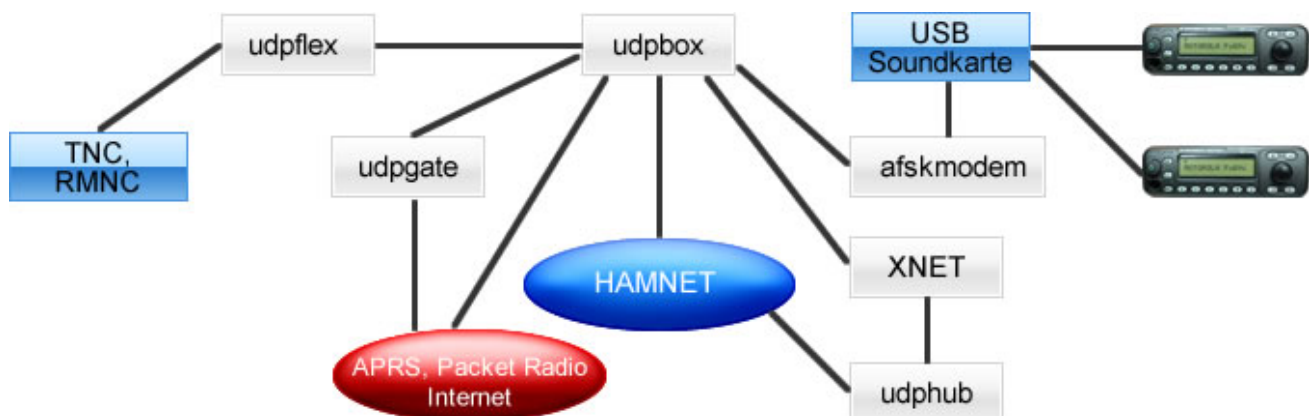

Help

If you need help on configuring the software packages you can contact OE5DXL on packet radio convers channel 501.

TCE Tinycore Linux Project englisch: Unterschied zwischen den Versionen

[Versionsgeschichte interaktiv durchsuchen](#)
[Visuell Wikitext](#)

Version vom 9. März 2015, 17:08 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
([→Help](#))
[← Zum vorherigen Versionsunterschied](#)

Version vom 7. August 2020, 09:51 Uhr (Quelltext anzeigen)
[OE2WAO](#) ([Diskussion](#) | [Beiträge](#))
[K](#)
[Zum nächsten Versionsunterschied →](#)

Zeile 1:	Zeile 1:
	[[Datei:Deutschland-flagge.gif]] Für die deutsche Version dieses Projekts [[TCE Tinycore Linux Projekt >>hier klicken<<]]
==Intro==	==Intro==
[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]	[[Bild:PPC.jpg thumb 500MHz LowPower industrial PC]]

Version vom 7. August 2020, 09:51 Uhr

 Für die deutsche Version dieses Projekts [>>hier klicken<<](#)

Inhaltsverzeichnis

1	Intro	15
2	Hardware	15
2.1	Connections and conversion of the used industrial pc	15
2.2	Soundcard	16
3	Software	16
3.1	Software schematic	16
4	Help	16

Intro


This hamradio software project is based on [TCE - Tinycore Linux](#), an embedded software system used on platforms like industrial pc, ALIX and others, and offers services and possibilities like

- packet radio,
- BBS,
- APRS,
- lightning log,
- small webserver,
- SVX-Link (Echolink)

especialy in networks like HAMNET and similar.

One goal is a minimum on material expenditure and also a minimal current consumption, followed by a maximum of features

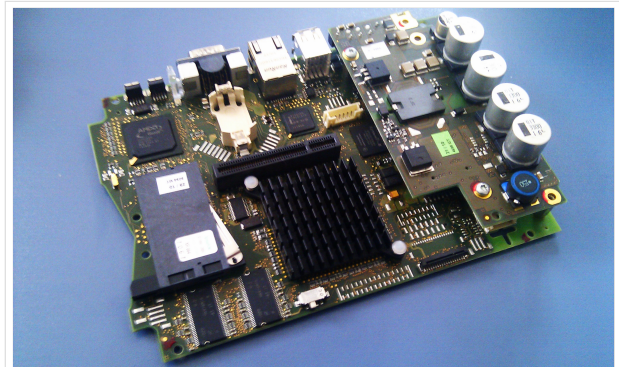More information on the hamradio TCE - tinycore linux project coming here soon




500MHz LowPower industrial PC

Hardware

DH2IW Wolfgang, OE2WAO Mike and OE5DXL Chris are doing first experiments with discarded industrial pc hardware, a 500MHz AMD Geode CPU with up to 256MB of RAM, and a minimal power input of <5Watt (for remaining stock ask [OE2WAO](#)).

But every other hardware platform like ALIX or similar will do.

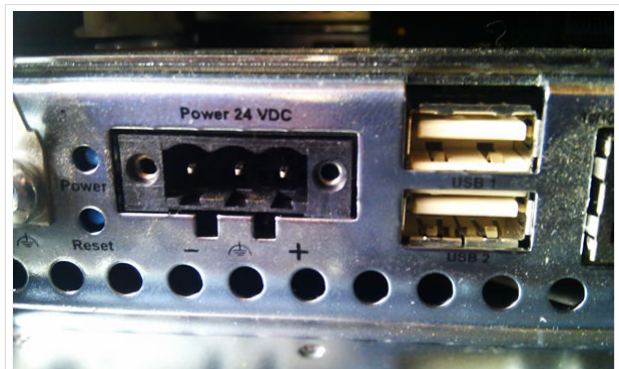The operating system is placed on a CF memory card (>32MB).



polarity industrial PC


A USB soundcard is used for operating AFSK /FSK modulation. One special character of working devices is a 3rd connector beside microphone and line out, the line in. Because these device are real stereo and make it possible to operate two separate channels on one sound card.

Connections and conversion of the used industrial pc

There are several connectors (COM, USB, network) on the frontside of our panels, as you can see. For correct polarity it is important to connent the + pole to the right pin of the 3pol power supply connector, the pin which is closer to the USB ports. The negative pole is the left pin.

The normal board supply is 24V.

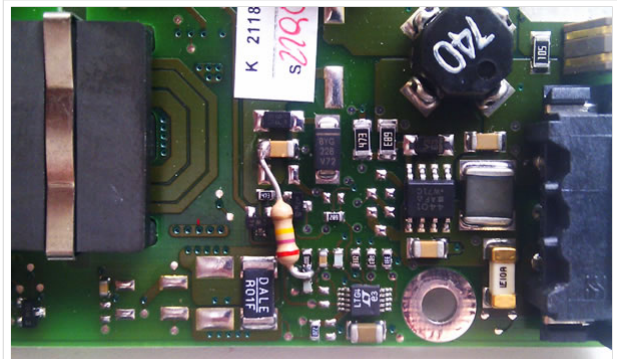That we can use it with our 12V power supply, we have to do a little modification. Just add a 270k Ohm resistor on the bottom side of the power supply as shown in the picture.



power supply conversion 12V

Soundcard


If there is no onboard sound available, you can use a USB soundcard instead. Suggested types you can find [here](#).

Software

A ready-to-use software image is located on the [OE2WAO Server](#) (e.g. tc455x-128.zip means version 4.55 with GUI on 128MB data drive)

There is also a version for raspberry pi hardware in test, and available soon.

Software schematic

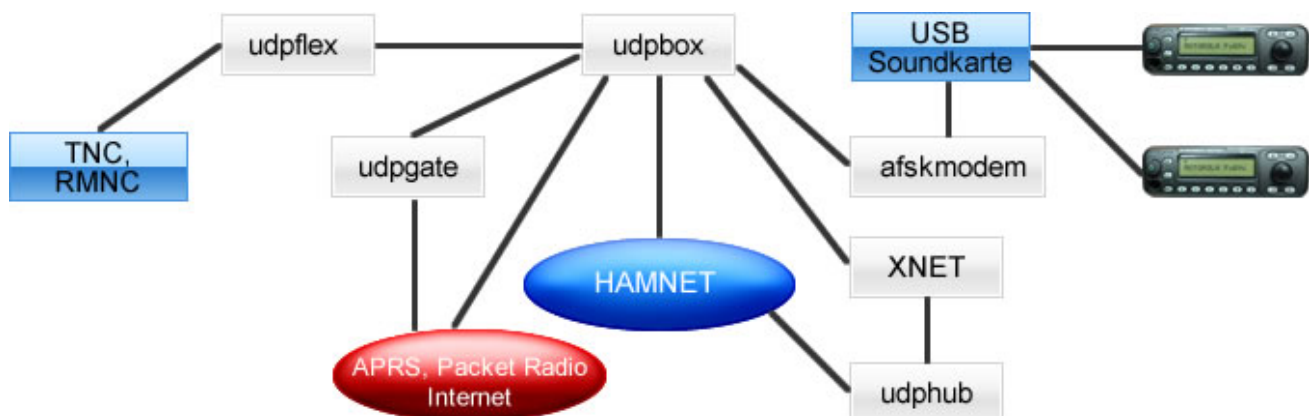

Help

If you need help on configuring the software packages you can contact OE5DXL on packet radio convers channel 501.